

CHOPPER DC TO DC CONVERTER



SATYAJIT SAHOO

LECTURER IN ELECTRICAL ENGINEERING



GOVERNMENT POLYTECHNIC, BOUDH

Government of Odisha


ସରକାରୀ ବହୁବୃତ୍ତି ଅନୁଷ୍ଠାନ, ବୌଦ୍ଧ

KEY TOPICS TO BE COVERED

- PRINCIPLE OF CHOPPER OPERATION (STEP DOWN CHOPPER)
- CONTROL STRATEGIES
- STEP UP CHOPPERS
- TYPES OF CHOPPER CIRCUITS
 - FIRST QUADRANT –TYPE A CHOPPER
 - SECOND QUADRANT –TYPE B CHOPPER
 - TWO QUADRANT TYPE A CHOPPER –TYPE C CHOPPER
 - TWO QUADRANT TYPE B CHOPPER –TYPE D CHOPPER
 - FOUR QUADRANT CHOPPER –TYPE E CHOPPER

PRINCIPLE OF CHOPPER OPERATION (STEP DOWN CHOPPER)

- A Chopper Is A High Speed On/Off Semiconductor Switch . It Connects Source To Load And Disconnects The Load From Source At A Fast Speed.
- During T_{on} , The Chopper Is On And Load Voltage (V_o) Is Equal To Source Voltage (V_s). The Load Current (I_o) Rises.
- During T_{off} , The Chopper Is Off And Load Current Flows Through The Freewheeling Diode. Load Terminals Are Short Circuited By Fd And Load Voltage (V_o) Is Zero. The Load Current (I_o) Decays.

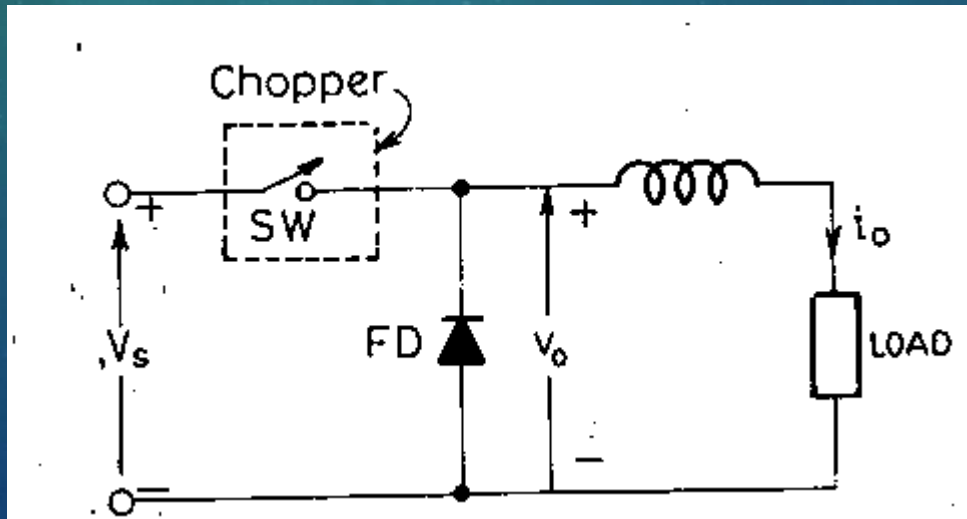


PRINCIPLE OF CHOPPER OPERATION (STEP DOWN CHOPPER)

$$V_0 = \frac{T_{on}}{T_{on} + T_{off}} V_s = \frac{T_{on}}{T} V = \alpha V_s$$

T_{on} = on-time ; T_{off} = off-time

$T = T_{on} + T_{off}$ = chopping period
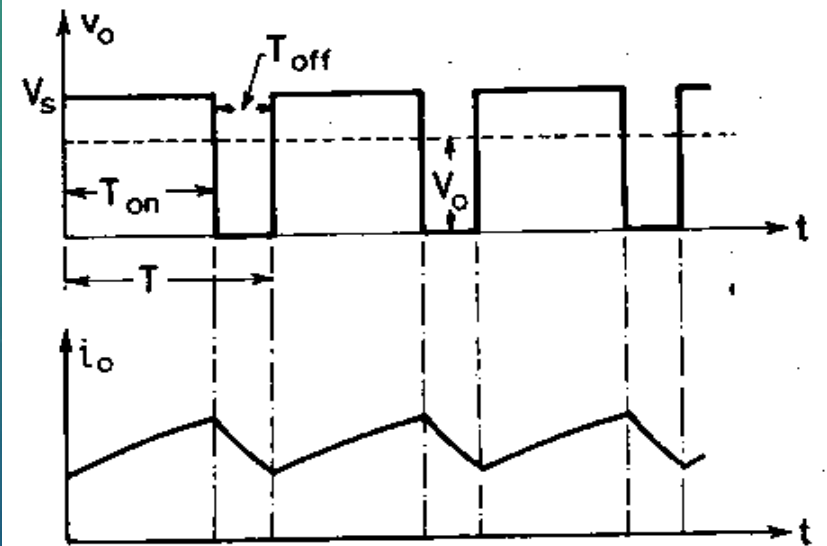
$$\alpha = \frac{T_{on}}{T} = \text{duty cycle}$$



$$V_0 = f \cdot T_{on} \cdot V_s$$


$$f = \frac{1}{T} = \text{chopping frequency}$$

CONTROL STRATEGIES

- TIME RATIO CONTROL
 - CONSTANT FREQUENCY SYSTEM
 - VARIABLE FREQUENCY SYSTEM
- CURRENT LIMIT CONTROL



CONSTANT FREQUENCY SYSTEM

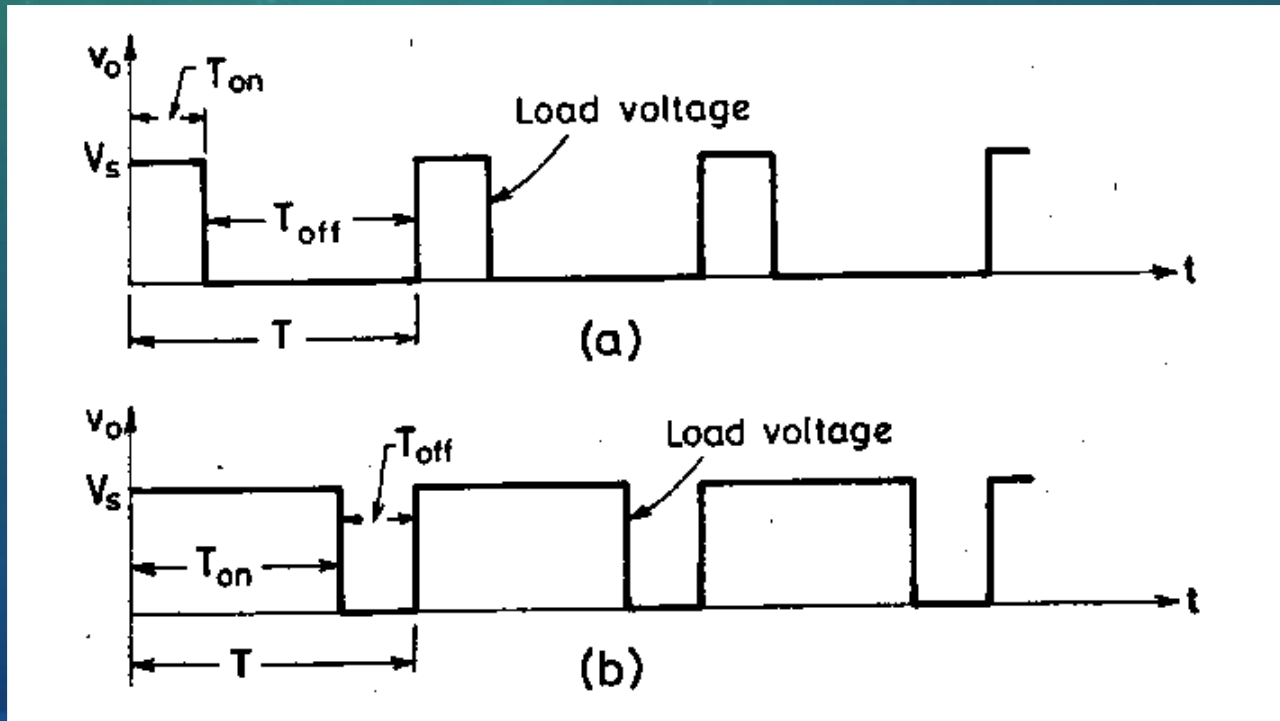- On Time Is Varied , Chopping Period Remains Same.
- Variation In T_{on} Means Adjustment Of Pulse Width So It Is Called Pulse Width Modulation (PWM).




VARIABLE FREQUENCY SYSTEM

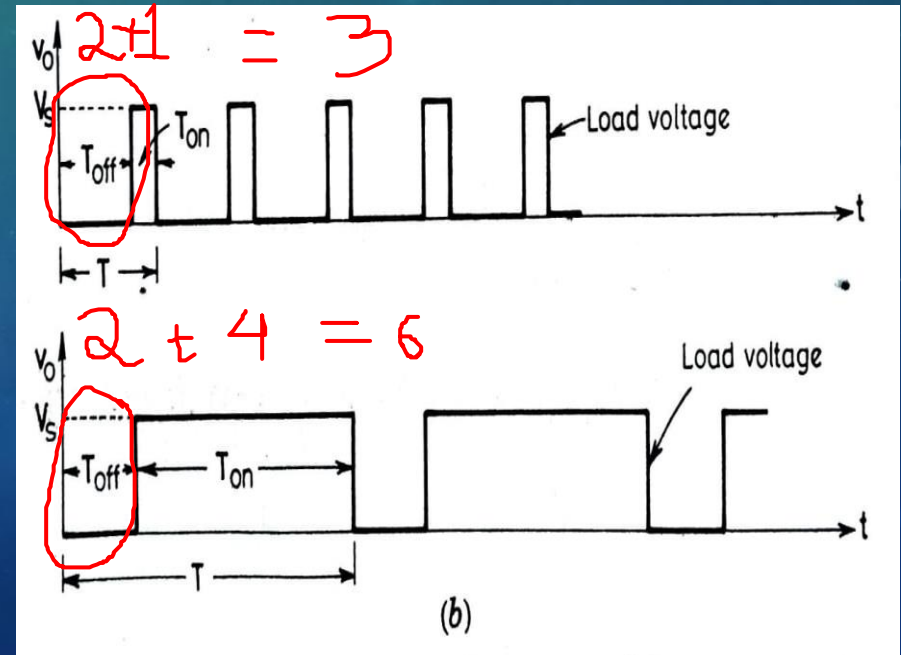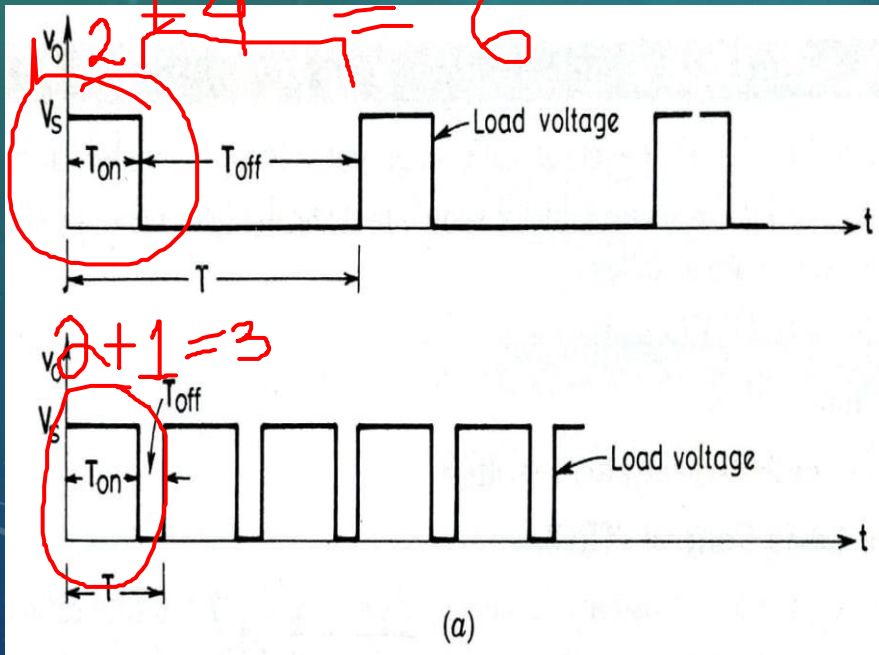- Chopping Frequency “ f ” (Or Chopping Period T) is varied and either
 - T_{on} is kept constant or
 - T_{off} is kept constant.



CURRENT LIMIT CONTROL

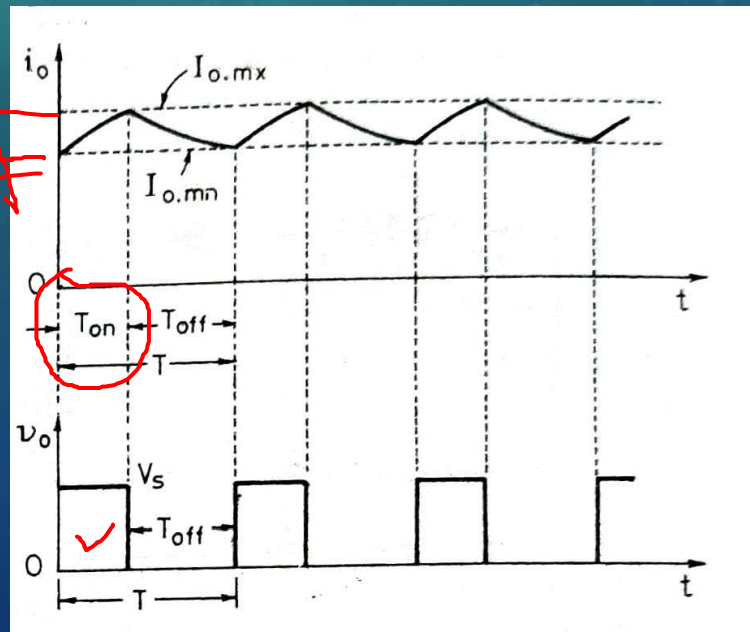- When Load Current Reaches The Upper Limit I_{max} , Chopper Is Switched Off.
- When It Falls To Lower Limit I_{min} , Chopper Is Switched On And Load Current Begins To Rise.



5A
3A

3 → 5
✓ ON

5 → 3
✓ off


STEP UP CHOPPER

- Average Output Voltage V_o Is Greater Than V_s .
- When The Chopper CH is On , The inductor stores energy.


$$V_o = 0 \text{ V}$$

- When The Chopper CH is Off , The inductor current cannot die down instantaneously, the current is forced to flow through the load for a time T_{off} .






$$V_o = V_s + L(di/dt)$$

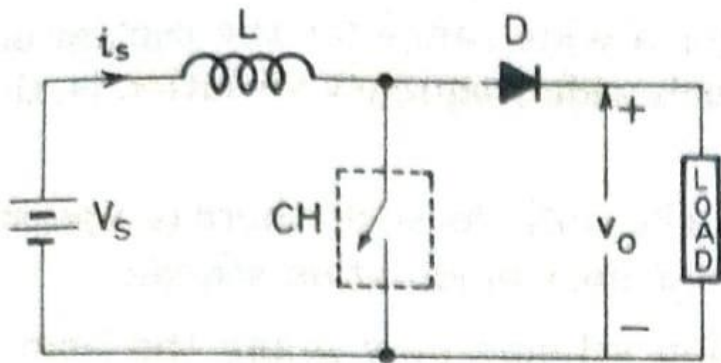

(a)


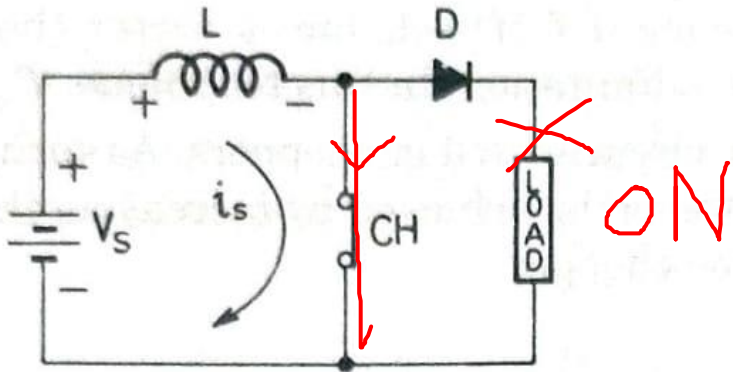


(b)

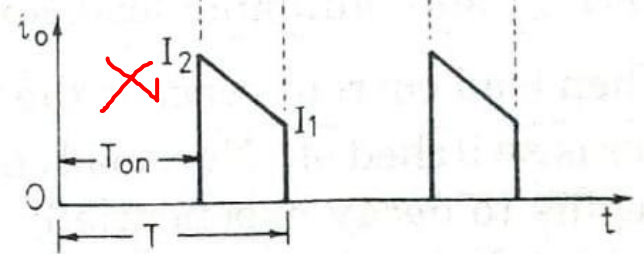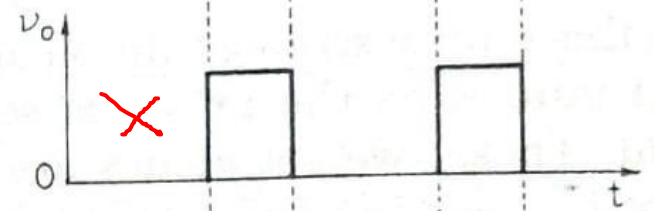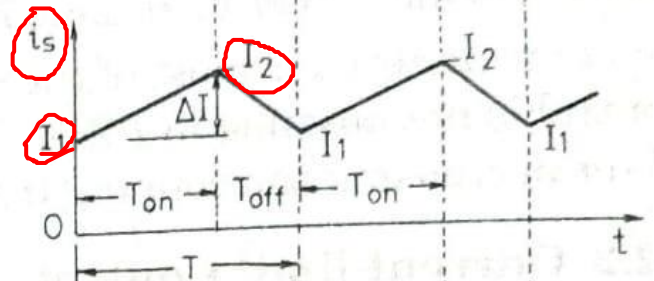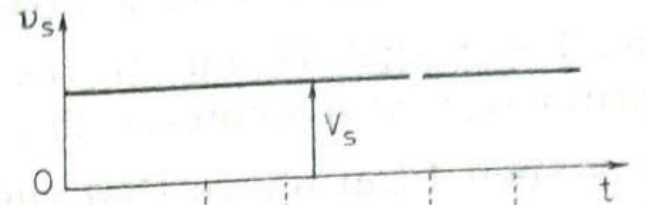
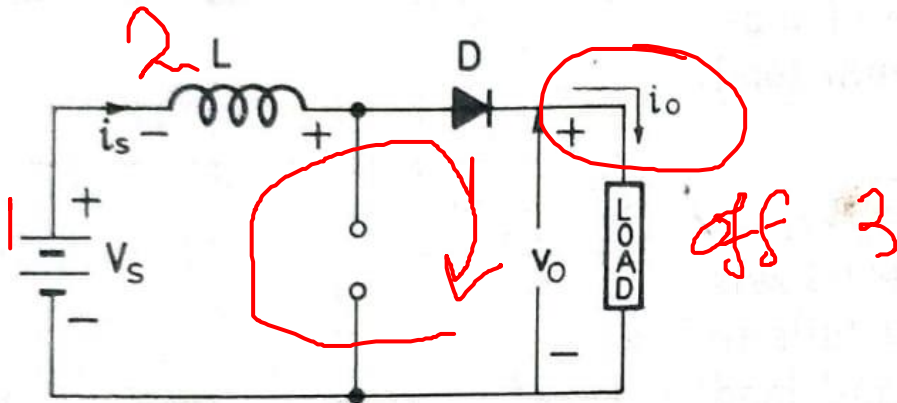


TYPES OF CHOPPER CIRCUITS

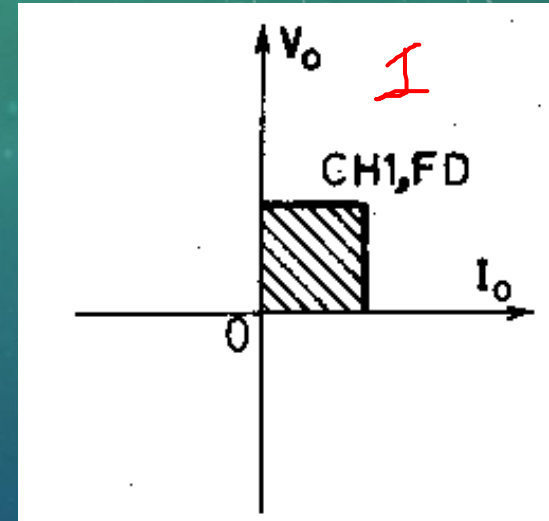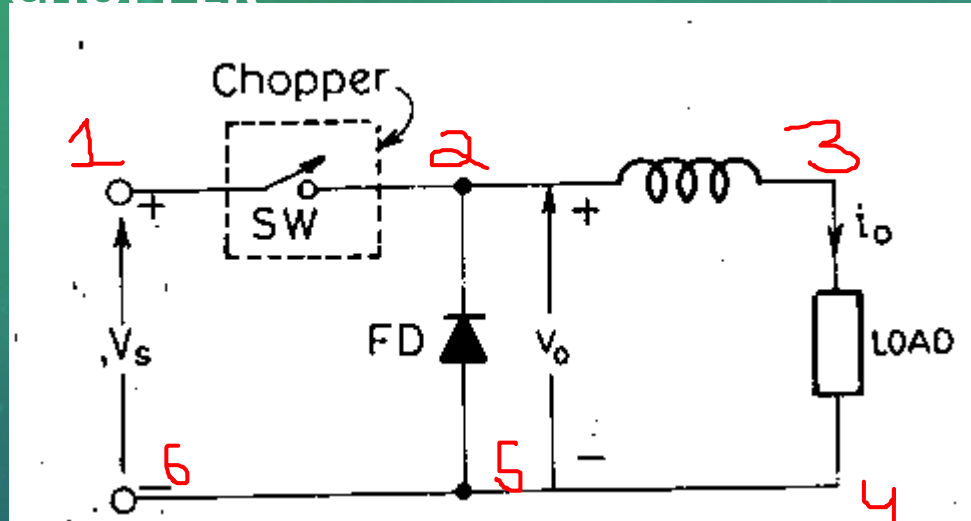
FIRST-QUADRANT –TYPE A CHOPPER – STEP DOWN CHOPPER



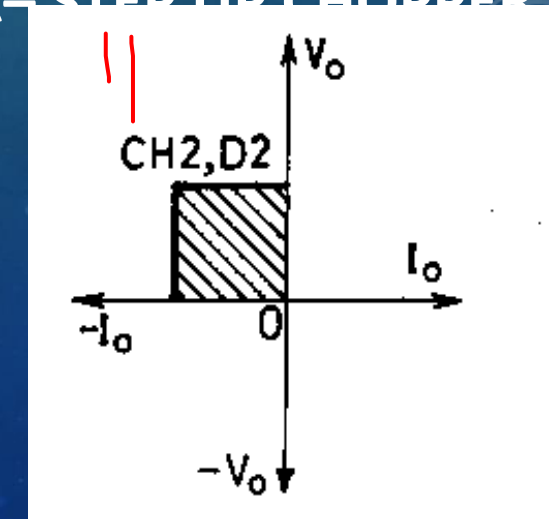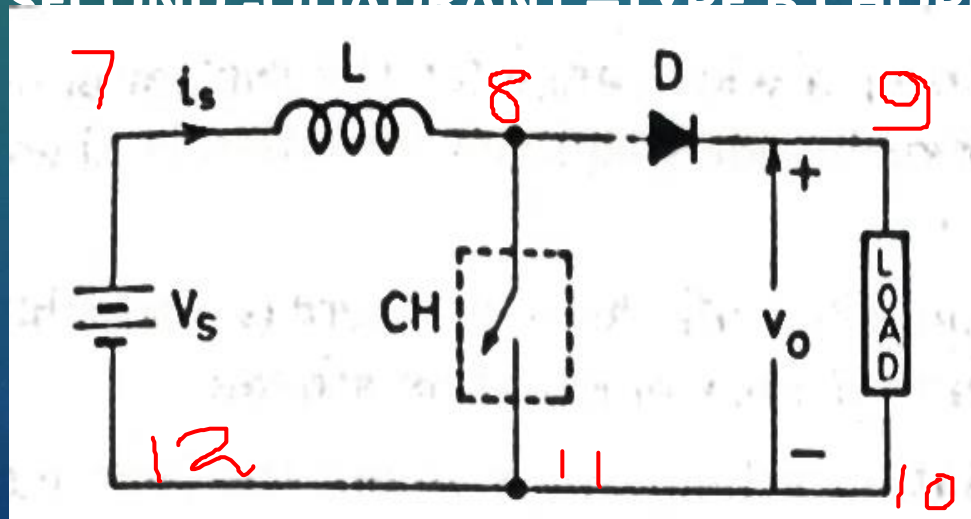SECOND-QUADRANT –TYPE B CHOPPER – STEP UP CHOPPER




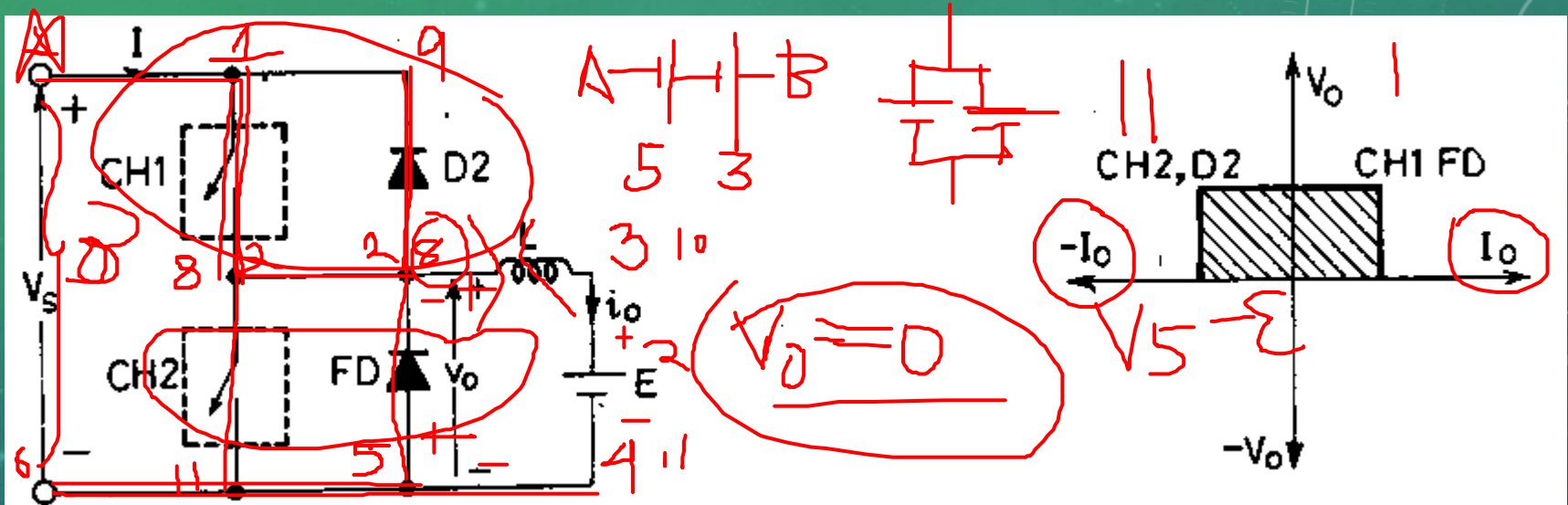TWO QUADRANT TYPE A CHOPPER – TYPE C CHOPPER



- OUTPUT VOLTAGE V_o IS ALWAYS POSITIVE BECAUSE OF FREEWHEELING DIODE ACROSS THE LOAD.
- CURRENT LIMIT CONTROL IS USED.
- WHEN D2 CONDUCTS OR CH1 IS ON, LOAD VOLTAGE $V_o = V_s (T_{ON})$
- WHEN FD CONDUCTS OR CH2 IS ON, LOAD VOLTAGE $V_o = 0 V (T_{OFF})$




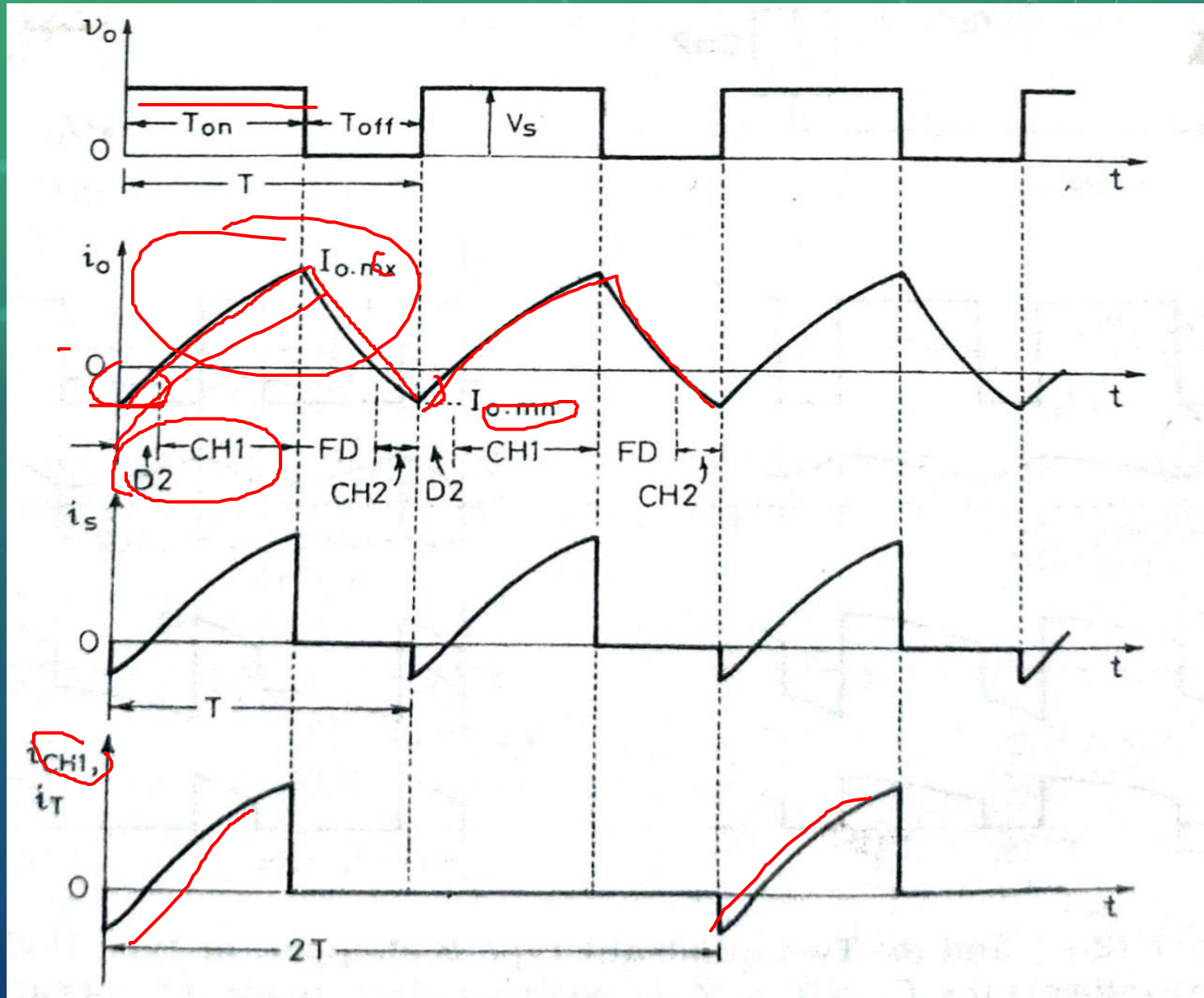
TWO QUADRANT TYPE A CHOPPER – TYPE C CHOPPER



TWO QUADRANT TYPE B CHOPPER – TYPE D CHOPPER

- When both the choppers CH1 and CH2 are on , $V_o = V_s$
- When both the choppers CH1 and CH2 are off and the diodes D1 and D2 are on , $V_o = -V_s$
- If T_{on} is greater than T_{off} , then the Average Output voltage V_o will be positive
- If T_{on} is less than T_{off} , then the Average Output voltage V_o will be negative
- Average Output Voltage (V_o can be positive or negative) but I_o is always positive.
- So the chopper works in two quadrants i.e. First and Fourth

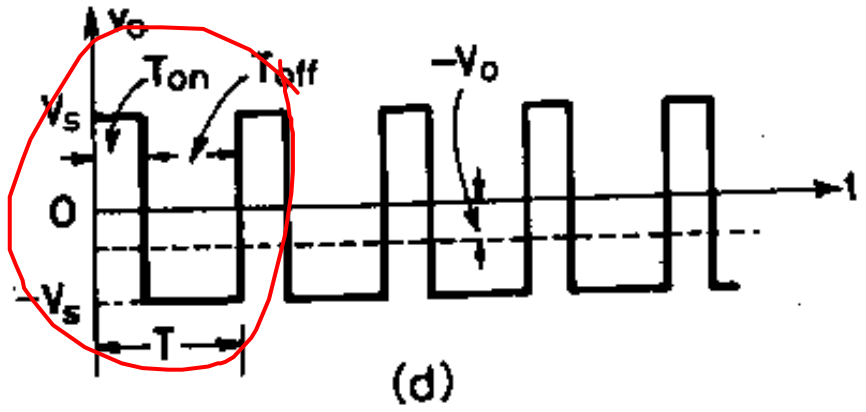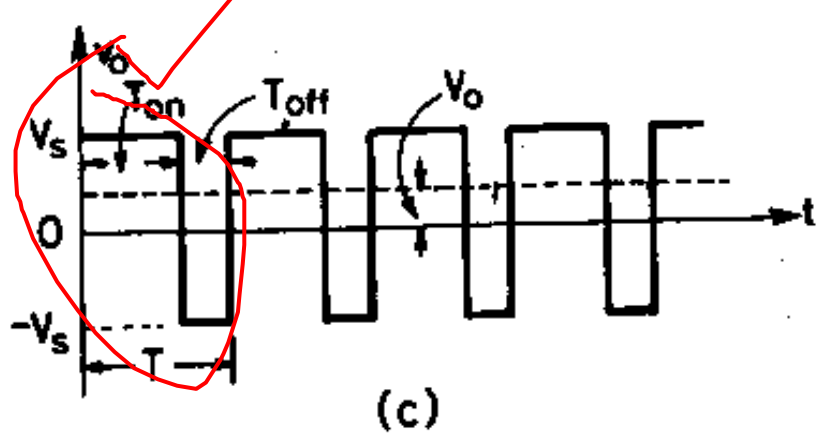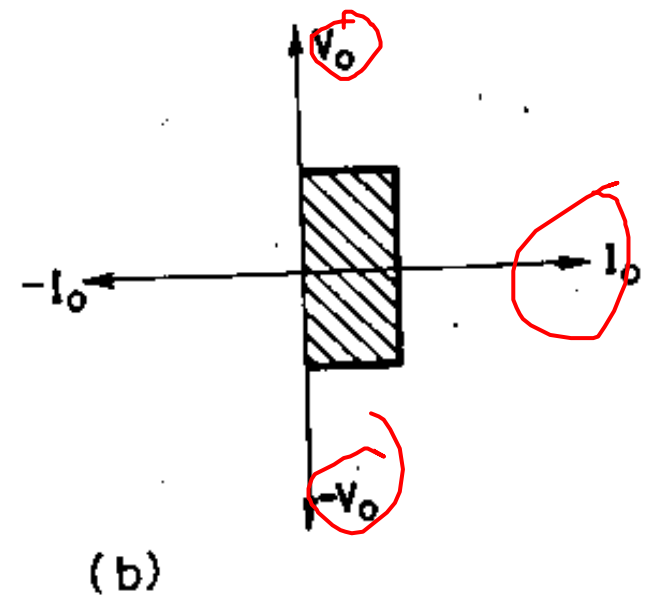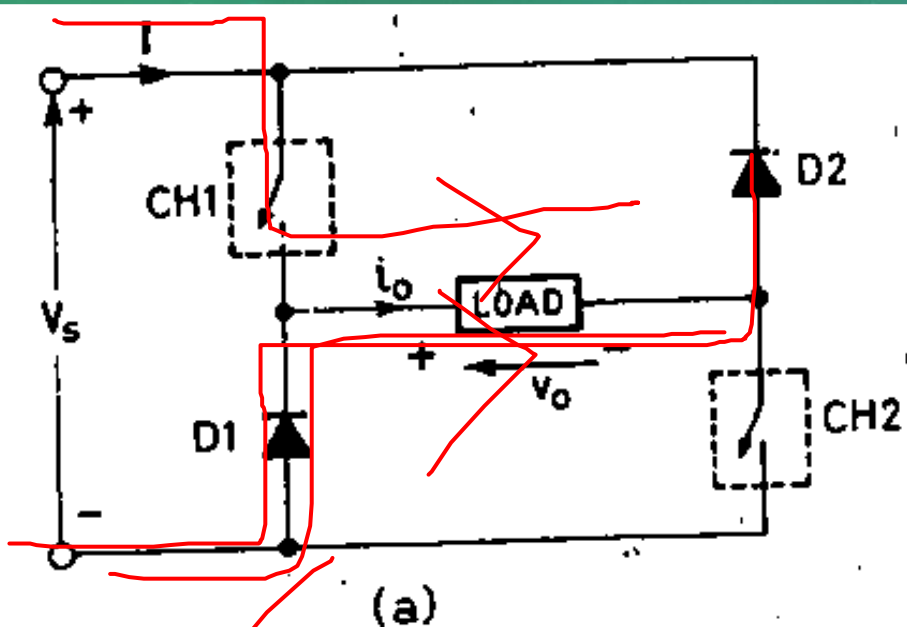TWO QUADRANT TYPE B CHOPPER – TYPE D CHOPPER



FOUR QUADRANT CHOPPER –TYPE E CHOPPER

- **First Quadrant:**

- CH4 is kept on , CH3 is kept off and CH1 operated , When CH1, CH4 on then $V_o = V_s$.
- When CH1 is off, positive current freewheels through CH4 , D2 .
- V_o and I_o both are positive , So operates in First quadrant .

- **Second Quadrant:**

- CH1 , CH3 and CH4 are off and CH2 is operated .
- With CH2 on , reverse current flows through L , CH2 , D4 , E and the inductor stores energy .
- When CH2 is off , current is feedback to source through D1 and D4 .
- As the output voltage is greater than source voltage so the current flows from load to source and I_o is negative. But voltage V_o is always positive , so operates in second quadrant .

FOUR QUADRANT CHOPPER –TYPE E CHOPPER


- **Third Quadrant:**

- CH1 is kept on , CH2 is kept off and CH3 operated , When CH2, CH3 on then $V_o = -V_s$.
- When CH3 is off, negative current freewheels through CH2 , D4 .
- V_o and I_o both are negative , So operates in Third quadrant .

- **Fourth Quadrant:**

- CH1 , CH2 and CH3 are off and CH4 is operated .
- With CH4 on , reverse current flows through L , CH4 , D2 , E and the inductor stores energy .
- When CH4 is off , current is feedback to source through D2 and D3 .
- As the output voltage is greater than source voltage so the current flows from load to source and V_o is negative. But Current I_o is always positive , so operates in fourth quadrant .

FOUR QUADRANT CHOPPER –TYPE E CHOPPER

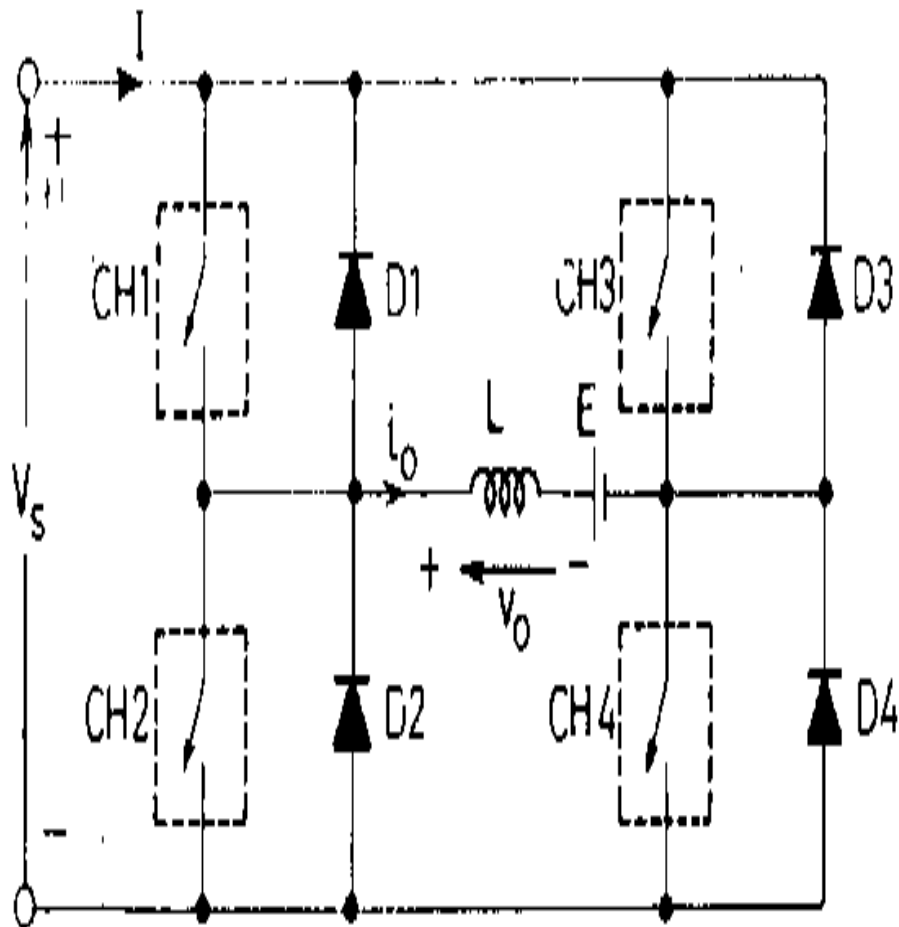

(a)

CH2 operated

CH2- D4 ; L_a stores energy

CH2 : off ; then D1-D4 conduct

CH3-CH2 : on

CH3 : off ; then CH2-D4 conduct

CH3 operated

CH1 operated


CH1-CH4 : on

CH1 : off ; then CH4-D2 conduct

CH4-D2 : L_a stores energy

CH4 : off ; then D2, D3 conduct

CH4 operated

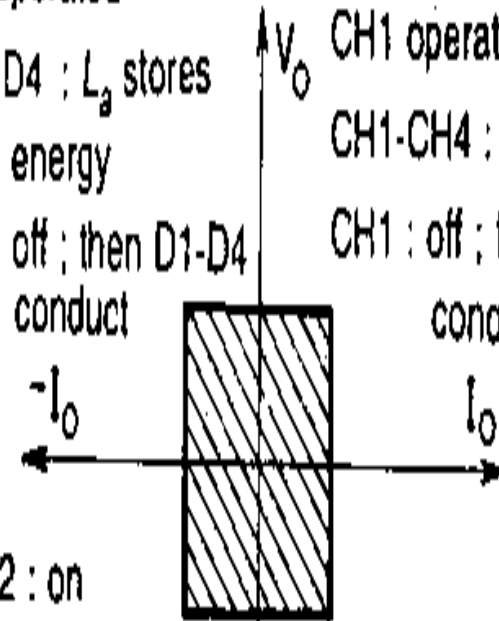

$-v_o$

(b)

The background is a blue gradient with faint technical diagrams and circular patterns. In the top right, there is a large circular diagram with a scale from 0 to 210 degrees. In the bottom right, there is a smaller circular diagram with a scale from 0 to 90 degrees. In the bottom left, there is another circular diagram with a scale from 0 to 90 degrees. The text "THANK YOU" is centered in a bold, yellow, sans-serif font.

THANK YOU