

# DC TO AC CONVERTER INVERTER



SATYAJIT SAHOO

LECTURER IN ELECTRICAL ENGINEERING



**GOVERNMENT POLYTECHNIC, BOUDH**

Government of Odisha

ସରକାରୀ ବହୁବୃତ୍ତି ଅନୁଷ୍ଠାନ, ବୌଦ୍ଧ

# **KEY TOPICS TO BE COVERED**

- **Classify inverters**
- **Single-phase bridge inverter**
- **Series inverter**
- **Parallel inverter**




# CLASSIFICATION OF INVERTERS


- Classification on basis of Connection of Semiconductor Devices.
  - Series inverter
  - Parallel inverter
  - Single-phase bridge inverter
    - Single-phase half bridge inverter
    - Single-phase full bridge inverter
- Classification on basis of Source
  - Current Source Inverter
  - Voltage Source Inverter

# SINGLE-PHASE BRIDGE INVERTER

- Single-phase half bridge inverter

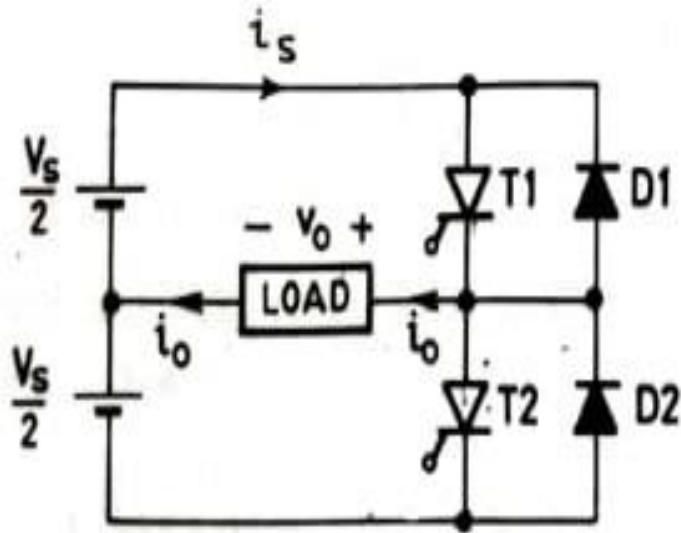

(a)

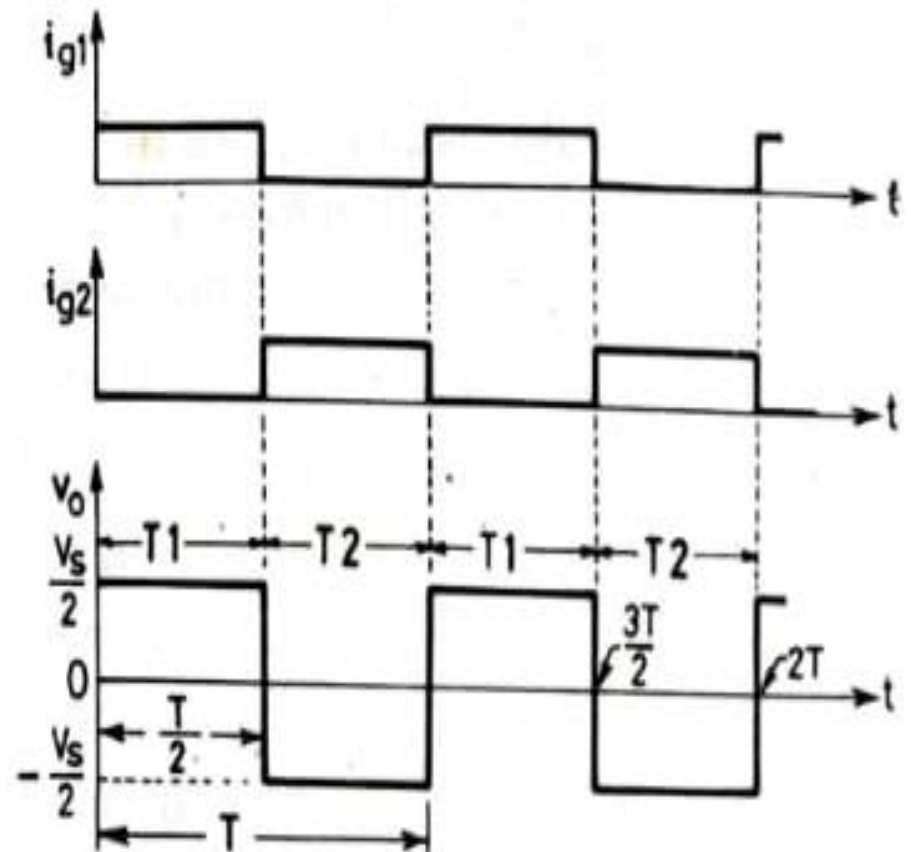


(b)




# SINGLE-PHASE BRIDGE INVERTER

- Single-phase full bridge inverter

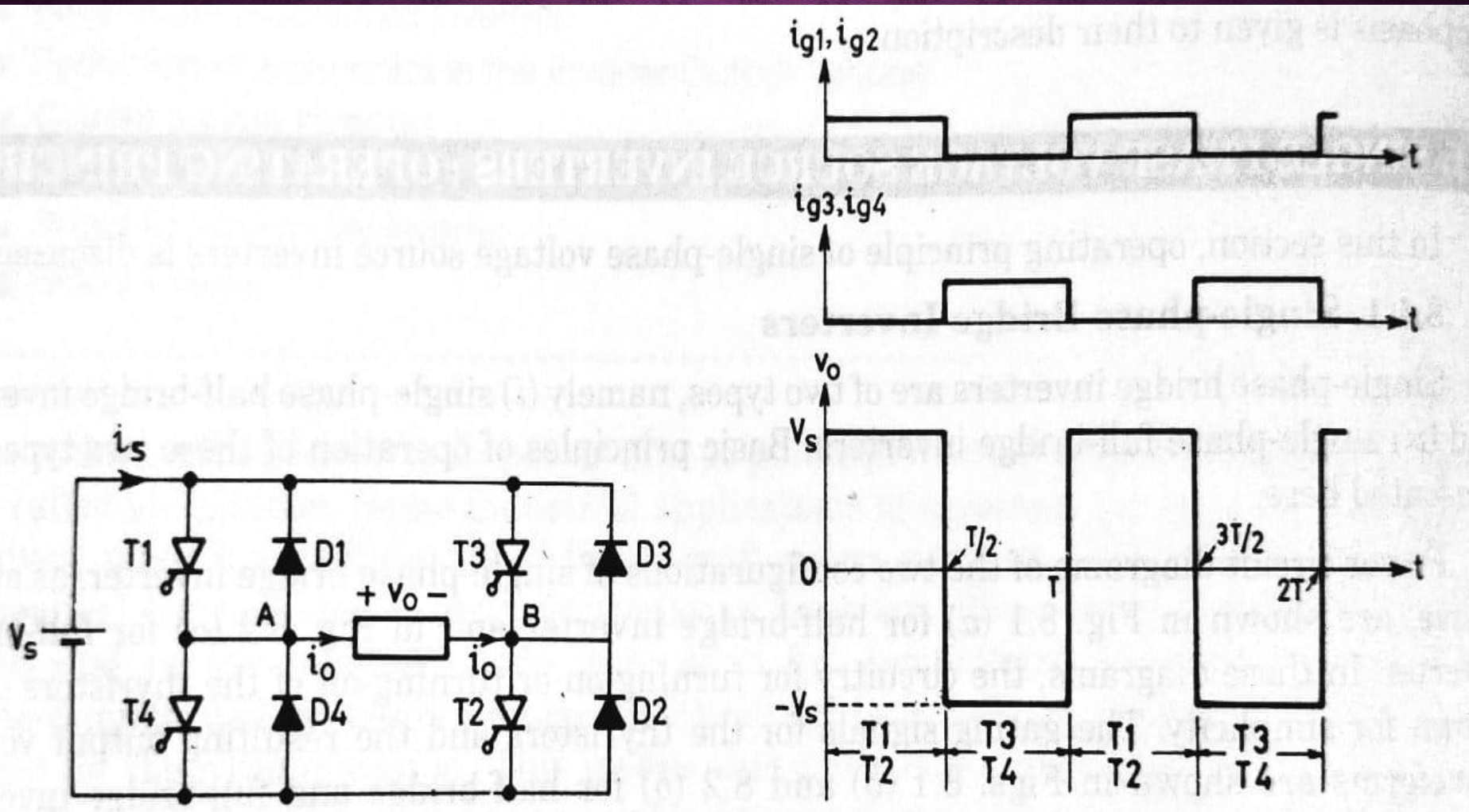
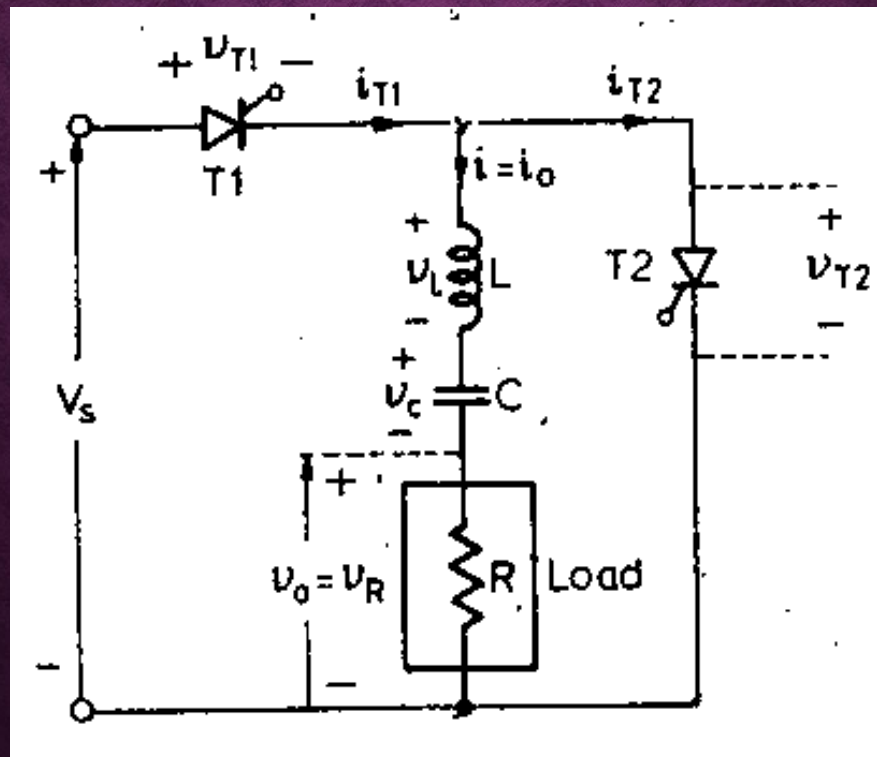
# SERIES INVERTER


- Inverters in which commutating components are permanently connected in series with load.
- The figure shows a basic series inverter in which the load resistance “R” is in series with commutating components L and C.





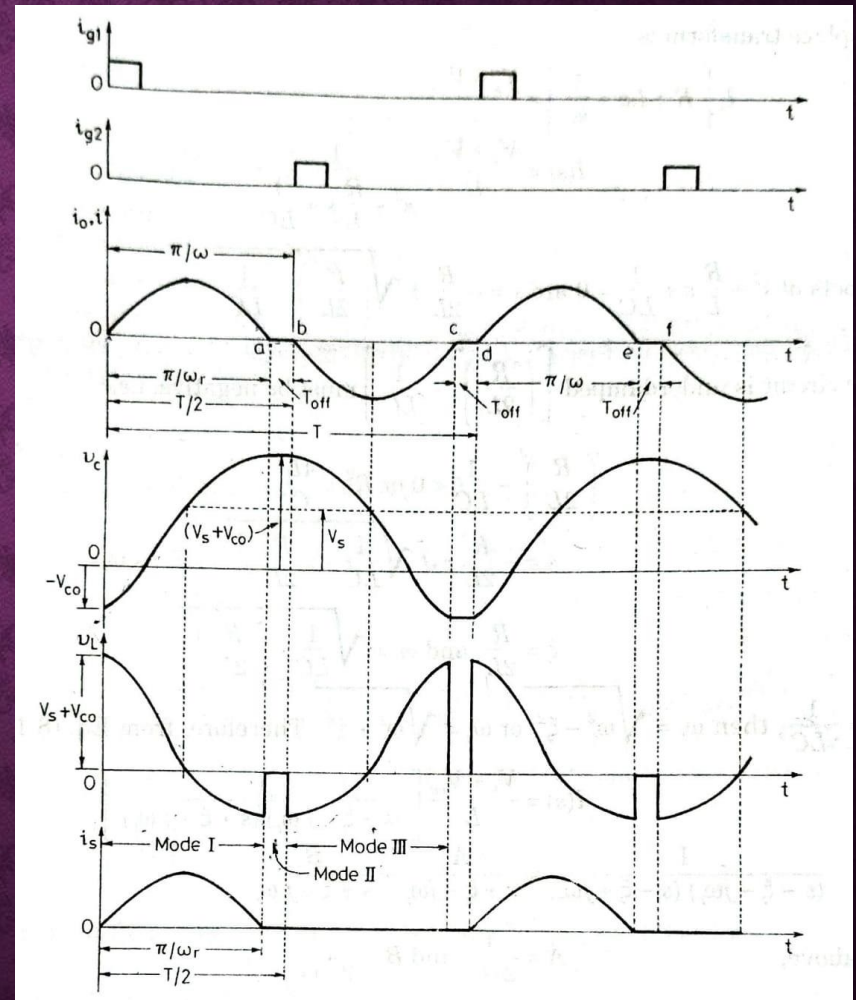
# SERIES INVERTER

- When T1 is turned on, with T2 off, Current  $i$  starts building up in the RLC circuit.
- At point 'a', T1 is turned off and some time must be provided to thyristor to regain its blocking capability.
- At point 'b', T2 is turned on. After T1 is off the upper part of the capacitor attains positive polarity and begins to discharge now and continues till point 'c'.
- After time  $cd$  must elapse for T2 to recover.
- At point 'd', T1 is again turned on and the process repeats.
- The time  $ab$  and  $cd$  is called circuit turn-off time or dead zone time.


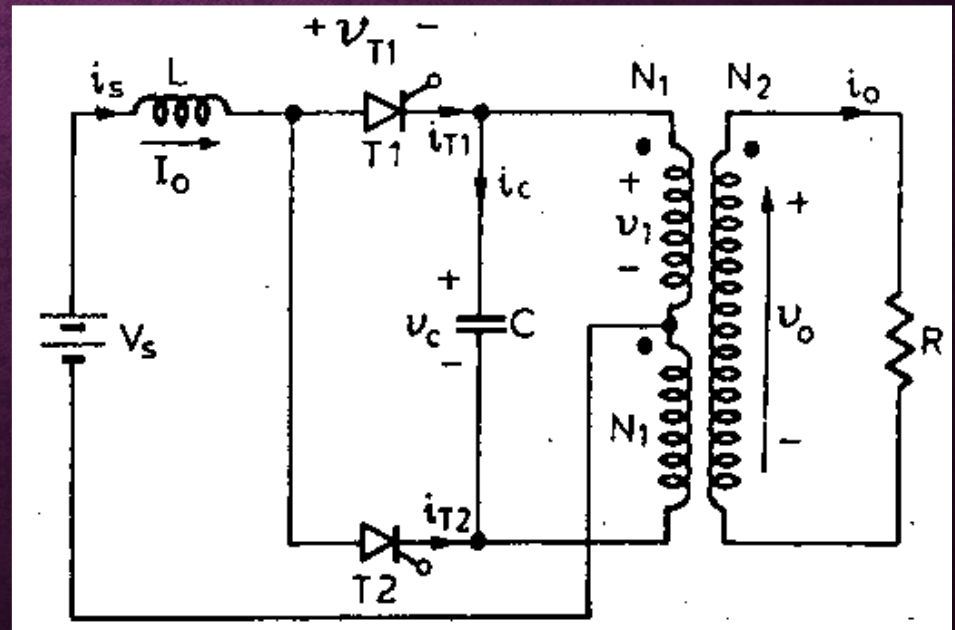
# PARALLEL INVERTER


- Inverters in which commutating components are permanently connected in parallel with load.
- It consists of two thyristors T1, T2 ,one inductor L, an output transformer and a commutating capacitor C.
- The turn ratio of transformer is 2 : 1 that can also written as 1:1 ::1.
- During working the capacitor C comes in parallel with the load via transformer so it is parallel inverter.
- It has three modes of operation.
  - Mode I
  - Mode II
  - Mode III




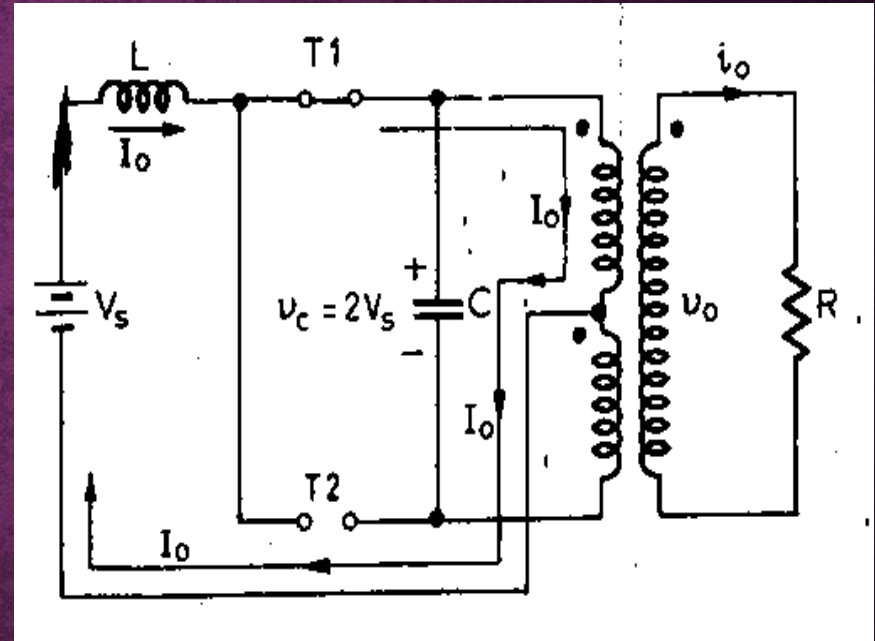
# PARALLEL INVERTER MODE-I

- T1 is conducting and a current flows in the upper half of primary. T2 is off.
- An emf  $V_s$  is induced in the upper half and so total emf in primary is equal to  $2V_s$ .
- This voltage charge the commutating capacitor C to a voltage  $2V_s$  with upper plate positive.
- Now the T2 is in forward blocking mode through T1 by the capacitor voltage ' $2V_s$ '.
- Here a current ' $I_o$ ' flows through  $V_s$ , L, T1 and upper half of primary.



During this mode

$$V_o = V_s$$


$$V_c = 2V_s$$

$$i_o = I_o$$

$$V_{T1} = 0$$
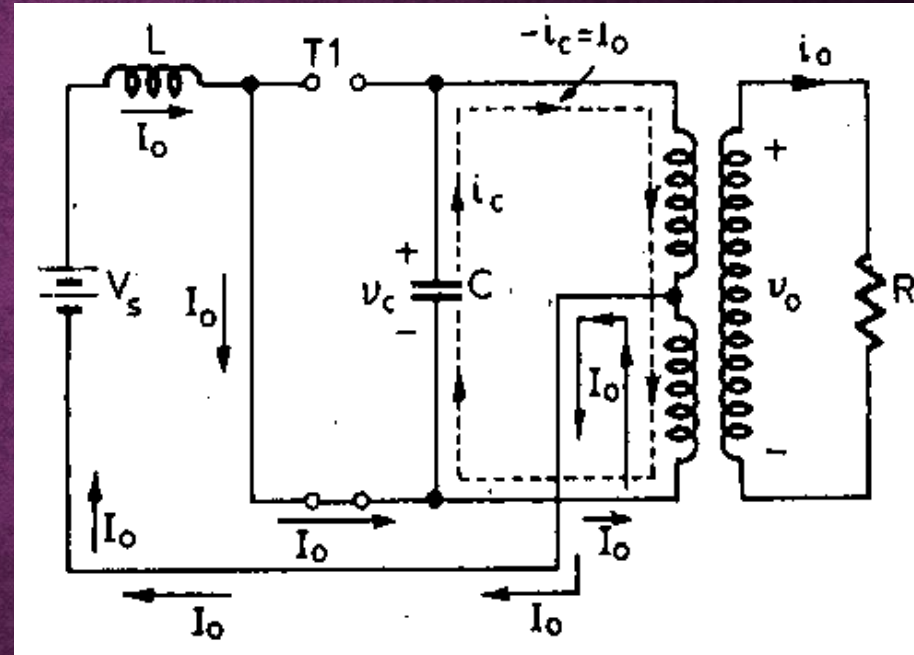
# PARALLEL INVERTER MODE-II

- T2 is turned on by applying gate pulse at  $t=0$ .
- The capacitor voltage  $2V_s$  appears as a reverse bias across T1 and gets turned off.
- A current  $I_o$  begins to flow through T2, lower half of primary winding. An emf  $-V_s$  is induced in the lower half and so total emf in primary is equal to  $-2V_s$ .
- This voltage charge the commutating capacitor C to a voltage  $-2V_s$  with lower plate positive at  $t=t_1$




During this mode

$$\begin{aligned} V_o &= -V_s \\ V_c &= -2V_s \\ i_o &= -I_o \\ V_{T2} &= 0 \end{aligned}$$


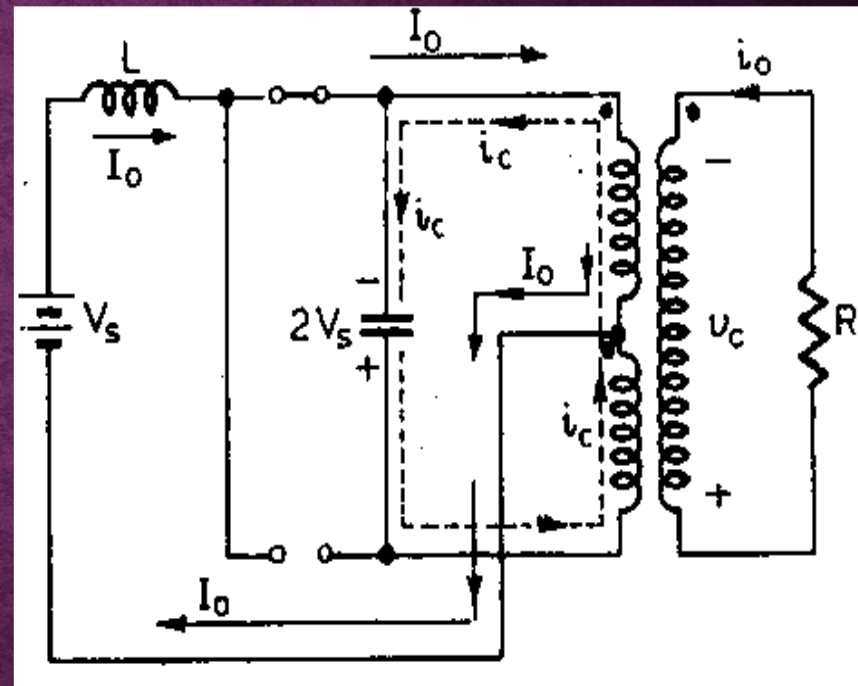
# PARALLEL INVERTER MODE-III

- When capacitor has charged to  $-2V_s$  with upper plate negative.
- The capacitor voltage  $2V_s$  appears as a reverse bias across T2 and gets turned off.
- A current  $I_o$  begins to flow through T1, upper half of primary winding. An emf  $V_s$  is induced in the lower half and so total emf in primary is equal to  $2V_s$ .
- This voltage charge the commutating capacitor C to a voltage  $2V_s$  with upper plate positive at  $t= T/2$



During this mode

$$V_o = V_s$$

$$V_c = 2V_s$$

$$i_o = I_o$$

$$V_{T1} = 0$$

**THANK YOU**